

---

# CS420/520 Computer Architecture I


## Single Cycle Datapath & Control

Dr. Xiaobo Zhou  
Department of Computer Science

---
 
## The Big Picture: Where are We Now?

- The Five Classic Components of a Computer




- Today's Topic: Datapath Design
 
## The Big Picture: The Performance Perspective

◦ Performance of a machine was determined by:

- Instruction count
- Clock cycle time
- Clock cycles per instruction




◦ Processor design (datapath and control) will determine:

- Clock cycle time
- Clock cycles per instruction

◦ In the next two lectures:

- Single cycle processor:
  - Advantage: One clock cycle per instruction
  - Disadvantage: long cycle time

## Review: Execution Cycle

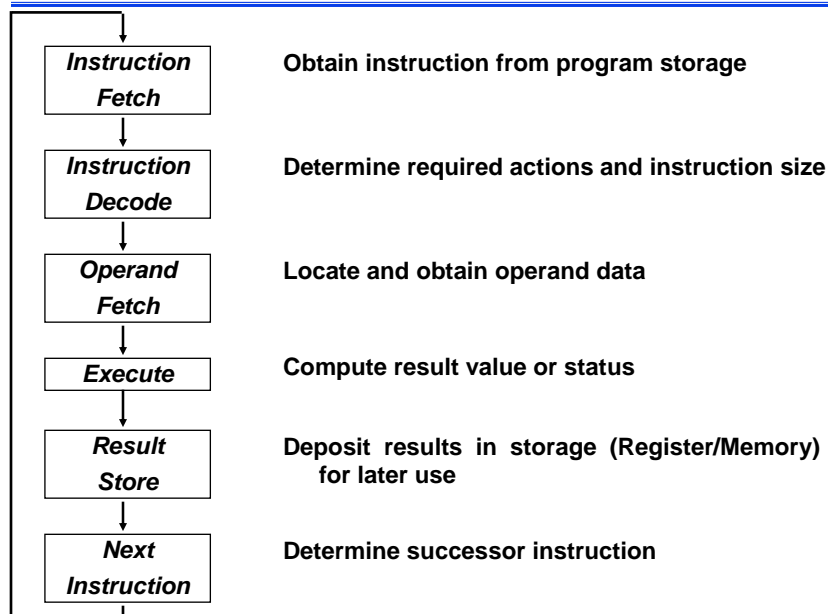


## Datapath Design Procedure

- **5 steps to design a processor**
  - 1. Analyze instruction set => datapath requirements
  - 2. Select set of datapath components & establish clock methodology
  - 3. Assemble datapath meeting the requirements
  - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
  - 5. Assemble the control logic
- **MIPS makes it easier**
  - Instructions same size/length
  - Source registers always in same place
  - Immediates same size, location
  - Operations always on registers/immediates
- **Single cycle datapath => CPI=1, CCT => long**
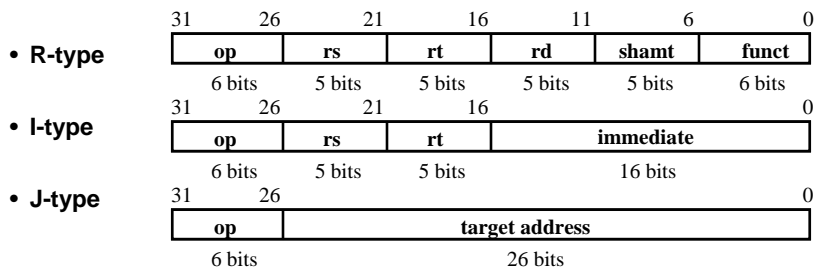
## The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. The three instruction formats:




- The different fields are:
  - op: operation of the instruction
  - rs, rt, rd: the source and destination register specifiers
  - shamt: shift amount
  - funct: selects the variant of the operation in the “op” field
  - address / immediate: address offset or immediate value
  - target address: target address of the jump instruction

## The MIPS Subset


◦ **ADD and subtract**

- add rd, rs, rt
- sub rd, rs, rt

 

◦ **OR Immediate:**

- ori rt, rs, imm16

 

◦ **LOAD and STORE**


- lw rt, rs, imm16
- sw rt, rs, imm16

◦ **BRANCH:**

- beq rs, rt, imm16

◦ **JUMP:**

- j target

 

## The Design is to Represent: ALU – Central Part of CPU

(1) **Functional Specification**

Inputs: 2 x 32 bit operands- A, B; 1 bit carry input- Cin.


Outputs: 1 x 32 bit result- S; 1 bit carry output- Co.

Operations: ADD (A plus B plus Cin), SUB (A minus B minus Cin), AND, OR, XOR

Performance: left unspecified for now!


(2) **Block Diagram**

Understand the data and control flows

 


## 4 Hardware Building Blocks

- AND gate ( $c = a \& b$ )

 


a	b	$c = a \& b$
0	0	0
1	0	0
0	1	0
1	1	1

- OR gate ( $c = a | b$ )

 


a	b	$c = a   b$
0	0	0
1	0	1
0	1	1
1	1	1

- Inverter ( $c = !a$ )

 

a	$c = !A$
0	1
1	0

 - Multiplexor  
if  $d=0$ ,  $c=a$ ;  
otherwise  $c=b$



d	c
0	a
1	b


CS420/520 datapath.9

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03
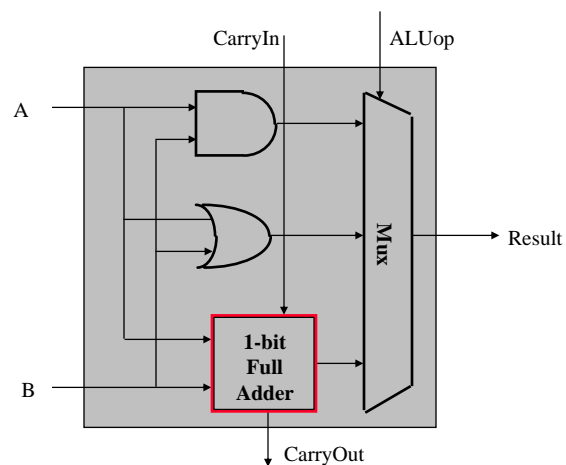
## A One Bit ALU

- This 1-bit ALU will perform AND, OR, and ADD




CS420/520 datapath.10

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03
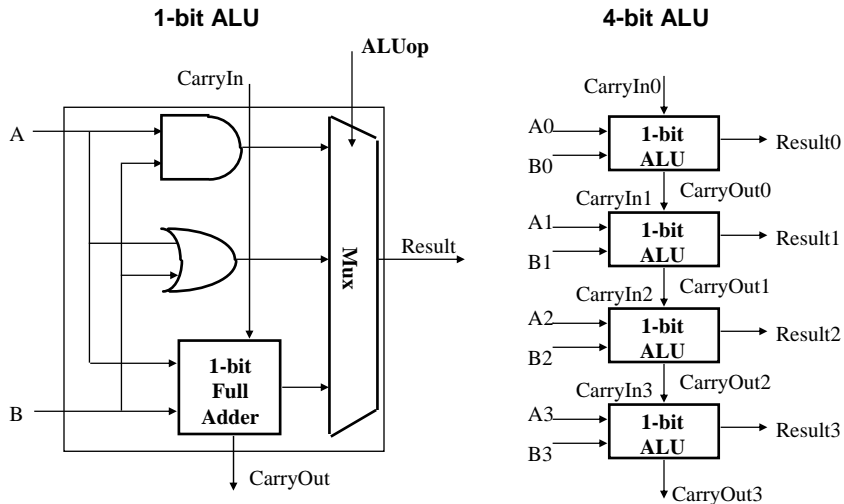
## A 1-bit ALU and a 4-bit ALU

- This 1-bit ALU will perform AND, OR, and ADD




CS420/520 datapath.11

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03
 
## How About Subtraction?

- Keep in mind the followings:
  - $(A - B)$  is the that as:  $A + (-B)$
  - 2's Complement: Take the inverse of every bit and add 1
- Bit-wise inverse of B is !B:
  - $A + !B + 1 = A + (!B + 1) = A + (-B) = A - B$




CS420/520 datapath.12

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03
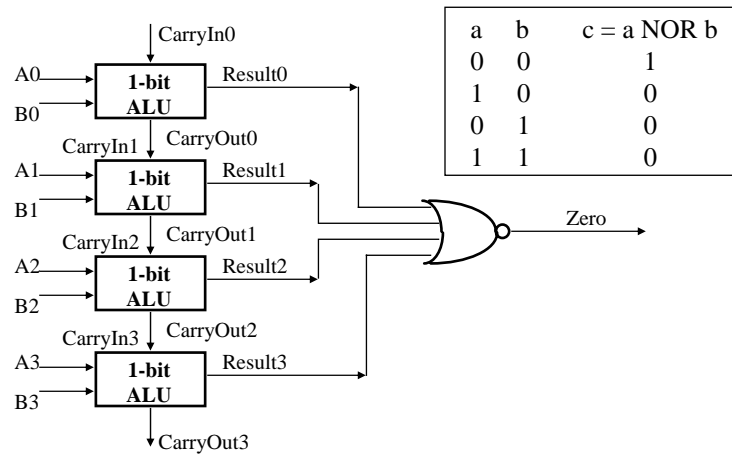
## Zero Detection Logic

- $A = B$  is the same as  $A - B = 0$
- Zero Detection Logic is just a one BIG NOR gate
  - Any non-zero input to the NOR gate will cause its output to be zero





CS420/520 datapath.13

UC. Colorado Springs

Adapted from ©UCB97 & ©UCB03
 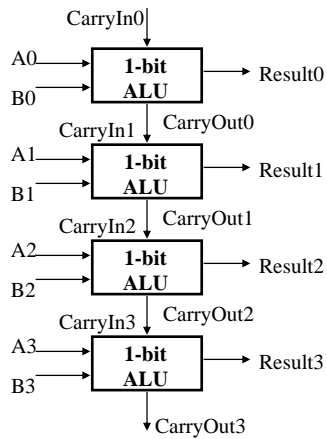
## The Disadvantage of Ripple Carry

- The adder we just built is called a “Ripple Carry Adder”
  - The carry bit may have to propagate from LSB to MSB
  - Worst case delay for a N-bit adder:  $2N$ -gate delay




CS420/520 datapath.14

UC. Colorado Springs

Adapted from ©UCB97 & ©UCB03
 
## Carry Select Header

- Consider building a 8-bit ALU
  - Simple: connects two 4-bit ALUs in series (ripple carry)




CS420/520 datapath.15

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03
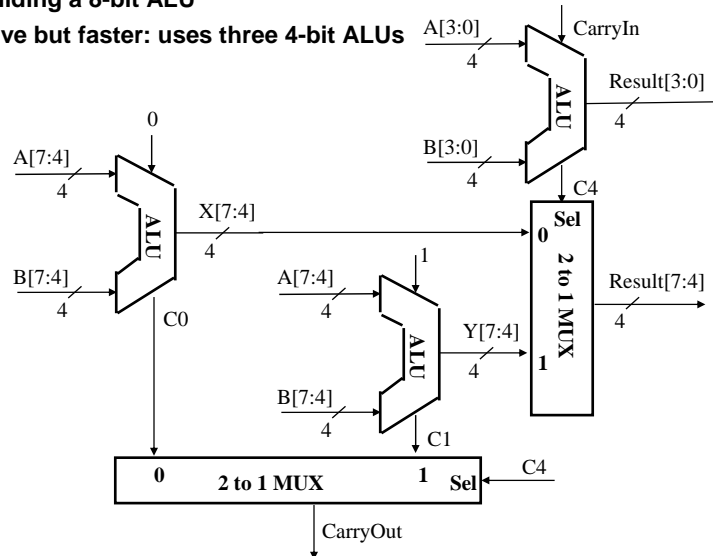
## Carry Select Header (Continue)

- Consider building a 8-bit ALU
  - Expensive but faster: uses three 4-bit ALUs



CS420/520 datapath.16


UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03




## Combinational Logic Elements


### ◦ Adder

 

### ◦ MUX

 

### ◦ ALU

 

CS420/520 datapath.17

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

## Storage Element: Register File

### ◦ Register File consists of 32 registers:


- Two 32-bit output busses: busA and busB
- One 32-bit input bus: busW

### ◦ Register is selected by:

- RA selects the register to put on busA
- RB selects the register to put on busB
- RW selects the register to be written via busW when Write Enable is 1
 
### ◦ Clock input (CLK)

- The CLK input is a factor ONLY during write operation
- During read operation, RF behaves as a combinational logic block:
  - RA or RB valid => busA or busB valid after "access time."




CS420/520 datapath.18

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

 
## Storage Element: Idealized Memory

- **Memory (idealized)**
  - One input bus: Data In
  - One output bus: Data Out
- **Memory word is selected by:**
  - Address selects the word to put on Data Out
  - Write Enable = 1: address selects the memory word to be written via the Data In bus
- **Clock input (CLK)**
  - The CLK input is a factor **ONLY** during write operation
  - During read operation, IM behaves as a combinational logic block:
    - Address valid => Data Out valid after “access time.”



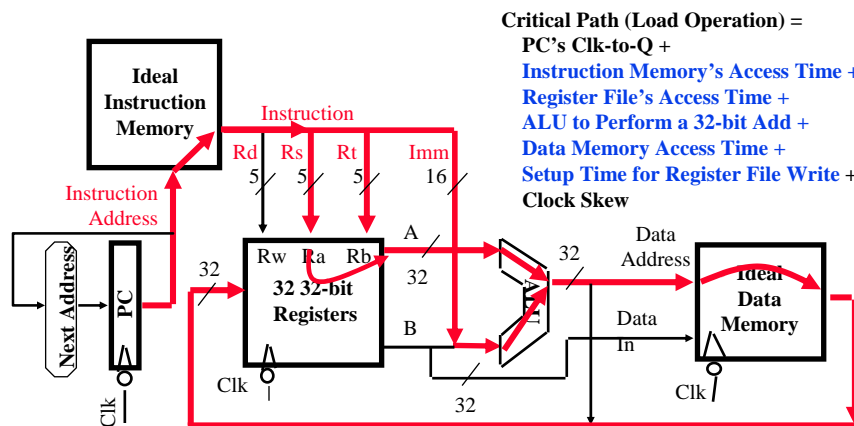
## An Abstract View of the Critical Path

- **Register file and ideal memory:**
  - The CLK input is a factor **ONLY** during write operation
  - During read operation, behave as combinational logic:
    - Address valid => Output valid after “access time.”




## Clocking Methodology

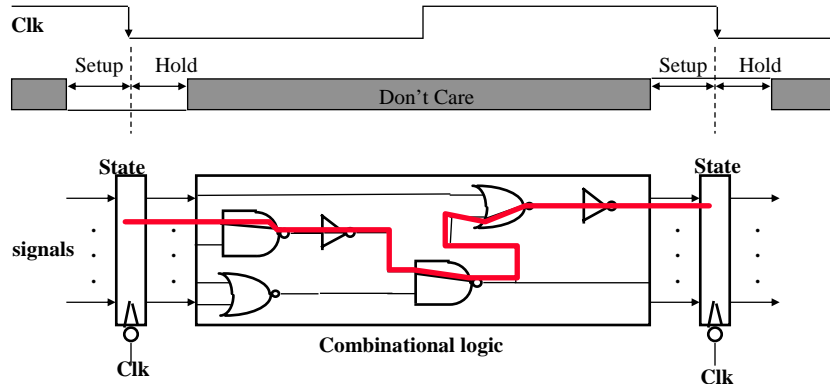


- A clocking methodology defines when signals can be read and written.
- For simplicity, we suppose an edge-triggered clocking methodology.
- All storage elements are clocked by the same clock edge
  - Edge-triggered: all stored values are updated on a clock edge
 
## Overview of the Instruction Fetch Unit

- The common operations
  - Fetch the Instruction:  $\text{mem}[\text{PC}]$
  - Update the program counter:
    - Sequential Code:  $\text{PC} \leftarrow \text{PC} + 4$
    - Branch and Jump  $\text{PC} \leftarrow$  "something else"




## The ADD Instruction

 

◦ **add rd, rs, rt**

- **mem[PC]**                      **Fetch the instruction from memory**
- **R[rd] <- R[rs] + R[rt]**      **The actual operation**
- **PC <- PC + 4**                  **Calculate the next instruction's address**

## The Subtract Instruction


 


◦ **sub rd, rs, rt**


- **mem[PC]**                      **Fetch the instruction from memory**
- **R[rd] <- R[rs] - R[rt]**      **The actual operation**
- **PC <- PC + 4**                  **Calculate the next instruction's address**
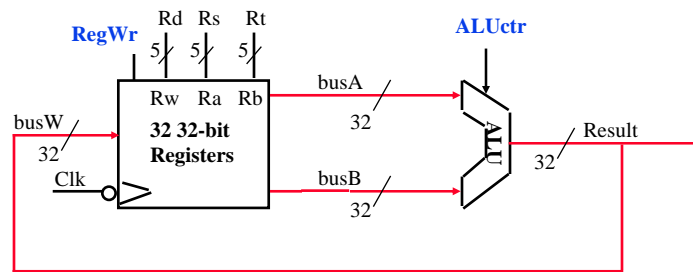 
## Datapath for Register-Register Operations


- $R[rd] \leftarrow R[rs] \text{ op } R[rt]$       Example: add rd, rs, rt
  - Ra, Rb, and Rw comes from instruction's rs, rt, and rd fields
  - ALUctr and RegWr: control logic after decoding the instruction



## The OR Immediate Instruction

 


 - ori rt, rs, imm16
  - mem[PC]      Fetch the instruction from memory
  - $R[rt] \leftarrow R[rs] \text{ or } \text{ZeroExt}(\text{imm16})$       The OR operation
  - $PC \leftarrow PC + 4$       Calculate the next instruction's address


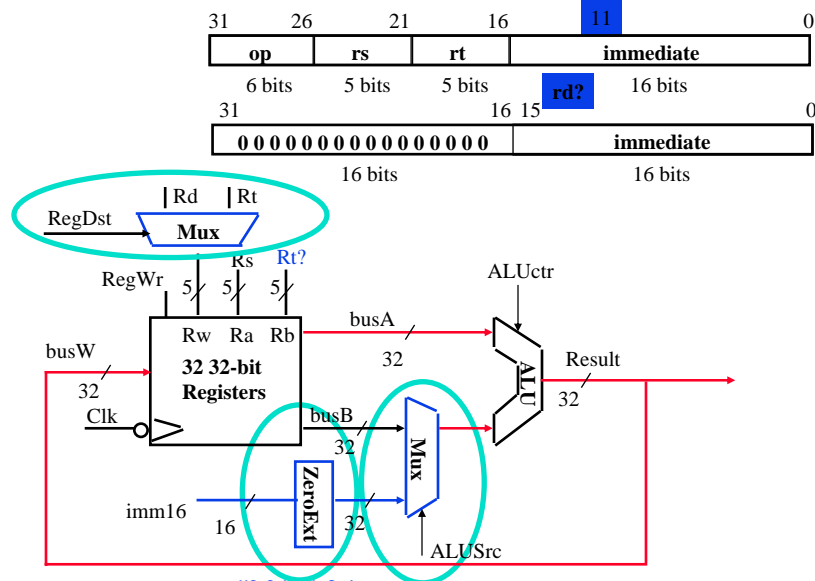
## Datapath for Logical Operations with Immediate


◦  $R[rt] \leftarrow R[rs] \text{ op ZeroExt}[imm16]$


 
## The Load Instruction


◦  $lw \quad rt, rs, imm16$

- $mem[PC]$  Fetch the instruction from memory
- $Addr \leftarrow R[rs] + \text{SignExt}(imm16)$  Calculate the memory address
- $R[rt] \leftarrow Mem[Addr]$  Load the data into the register
- $PC \leftarrow PC + 4$  Calculate the next instruction's address



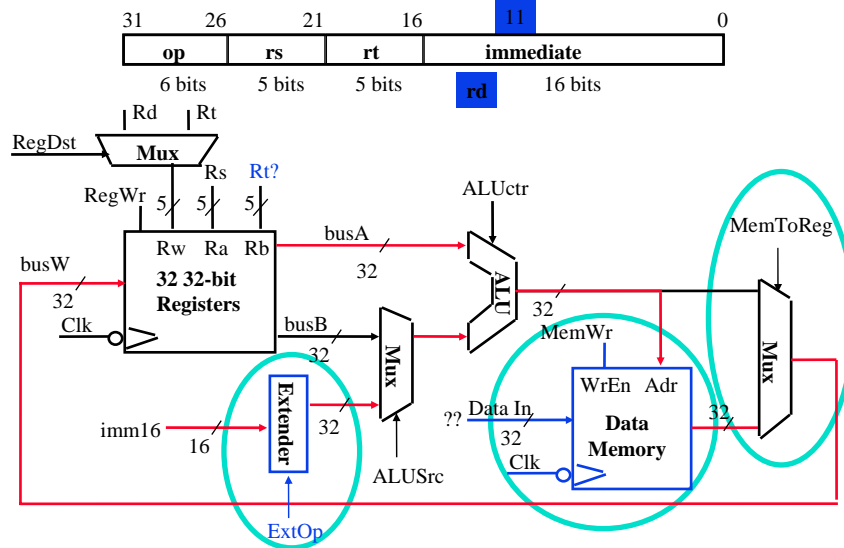
## Datapath for Load Operations

◦  $R[rt] \leftarrow \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$  Example: lw rt, rs, imm16



## The Store Instruction

 


◦ sw rt, rs, imm16

- mem[PC] Fetch the instruction from memory
- $\text{Addr} \leftarrow R[rs] + \text{SignExt}(\text{imm16})$  Calculate the memory address
- $\text{Mem}[\text{Addr}] \leftarrow R[rt]$  Store the register into memory
- $\text{PC} \leftarrow \text{PC} + 4$  Calculate the next instruction's address
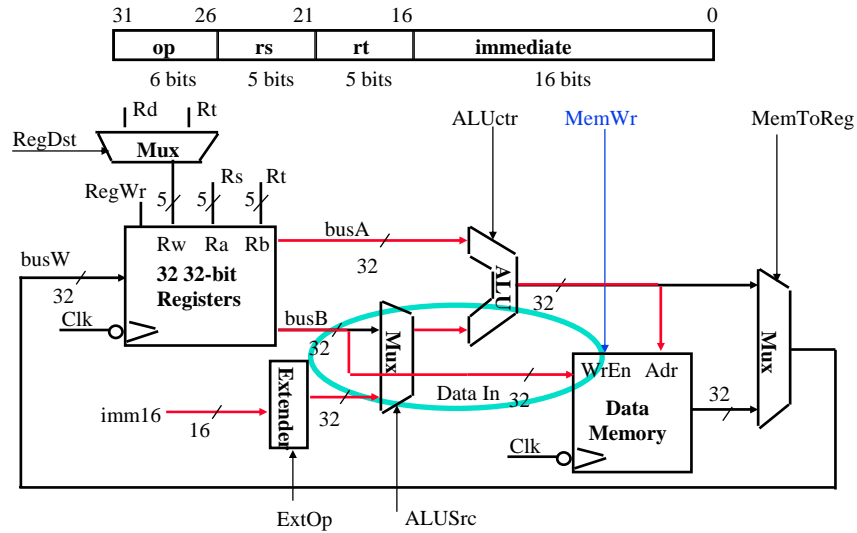
## Datapath for Store Operations

- $\text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}] \leftarrow R[\text{rt}]]$  Example: `sw rt, rs, imm16`




CS420/520 datapath.31

UC. Colorado Springs

Adapted from ©UCB97 & ©UCB03

## The Branch Instruction

 

- `beq rs, rt, imm16`

- `mem[PC]` Fetch the instruction from memory
- `Cond ← R[rs] - R[rt]` Calculate the branch condition
- if (COND eq 0) Calculate the next instruction's address
  - `PC ← PC + 4 + ( SignExt(imm16) x 4 )`
- else
  - `PC ← PC + 4`

CS420/520 datapath.32

UC. Colorado Springs


Adapted from ©UCB97 & ©UCB03



## Datapath for Branch Operations

◦ `beq rs, rt, imm16`

We need to compare Rs and Rt!

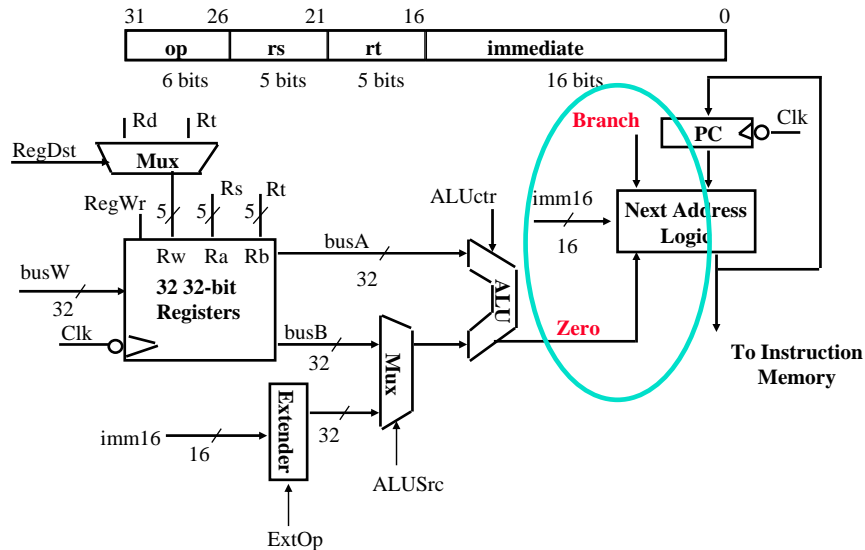


## Binary Arithmetics for the Next Address

- In theory, the PC is a 32-bit byte address into the instruction memory:
  - Sequential operation:  $PC\langle 31:0 \rangle = PC\langle 31:0 \rangle + 4$
  - Branch operation:  $PC\langle 31:0 \rangle = PC\langle 31:0 \rangle + 4 + \text{SignExt}[\text{Imm16}] * 4$
- The magic number “4” always comes up because:
  - The 32-bit PC is a byte address
  - And all our instructions are 4 bytes (32 bits) long
- In other words:
  - The 2 LSBs of the 32-bit PC are always zeros
  - There is no reason to have hardware to keep the 2 LSBs
- In practice, we can simplify the hardware by using a 30-bit  $PC\langle 31:2 \rangle$ :
  - Sequential operation:  $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1$
  - Branch operation:  $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1 + \text{SignExt}[\text{Imm16}]$
  - In either case: Instruction Memory Address =  $PC\langle 31:2 \rangle$  concat “00”
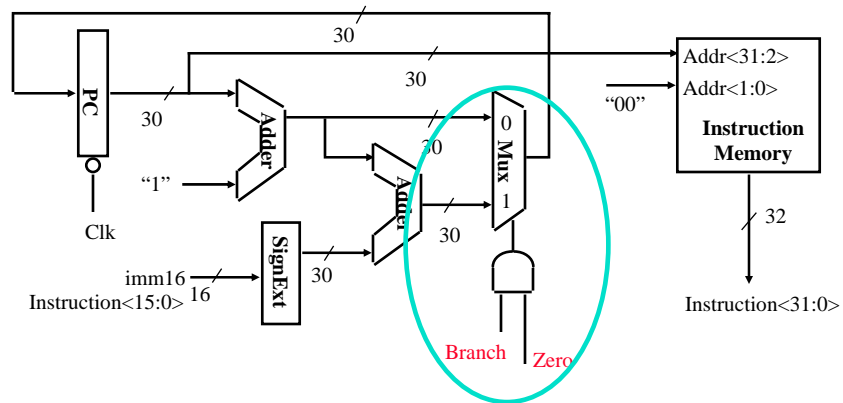
## Next Address Logic: Expensive and Fast Solution

- Using a 30-bit PC:
  - Sequential operation:  $PC_{<31:2>} = PC_{<31:2>} + 1$
  - Branch operation:  $PC_{<31:2>} = PC_{<31:2>} + 1 + \text{SignExt}[Imm16]$
  - In either case: Instruction Memory Address =  $PC_{<31:2>}$  concat "00"




CS420/520 datapath.35

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03
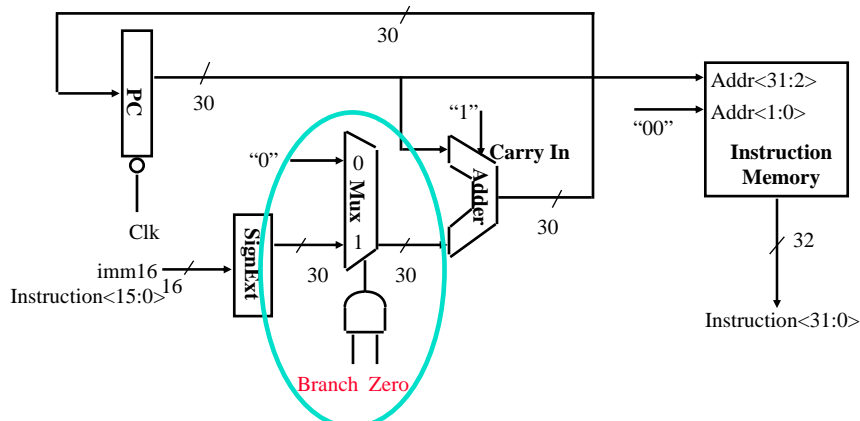
## Next Address Logic: Cheap and Slow Solution

- Why is this slow?
  - Cannot start the address add until Zero (output of ALU) is valid
- Does it matter that this is slow in the overall scheme of things?
  - Probably not here. Critical path is the load operation.



CS420/520 datapath.36


UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03


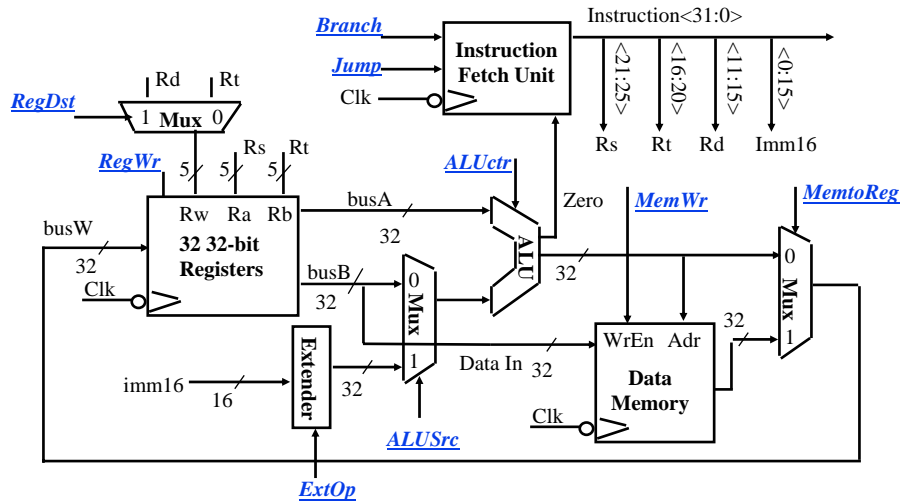
## Putting it All Together: A Single Cycle Datapath

- We have everything except control signals (underlined>), to be continued ...



CS420/520 datapath.39

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

## Summary of Datapath Design

- **5 steps to design a processor**
  - 1. Analyze instruction set => datapath requirements
  - 2. Select set of datapath components & establish clock methodology
  - 3. Assemble datapath meeting the requirements
  - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
  - 5. Assemble the control logic
- **MIPS makes it easier**
  - Instructions same size
  - Source registers always in same place
  - Immediates same size, location
  - Operations always on registers/immediates
- Single cycle datapath => CPI=1, CCT => long
- **What is next?: implementing control**


CS420/520 datapath.40

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

 
## The Big Picture: Where are We Now?

- The Five Classic Components of a Computer



- Topic: Designing the Control for the Single Cycle Datapath

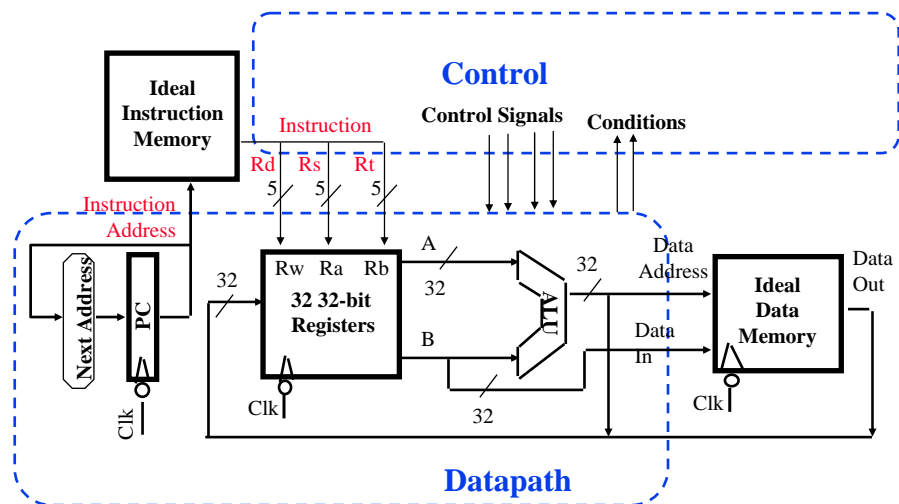
## An Abstract View of the Control Implementation







 
## The Single Cycle Datapath during Or Immediate



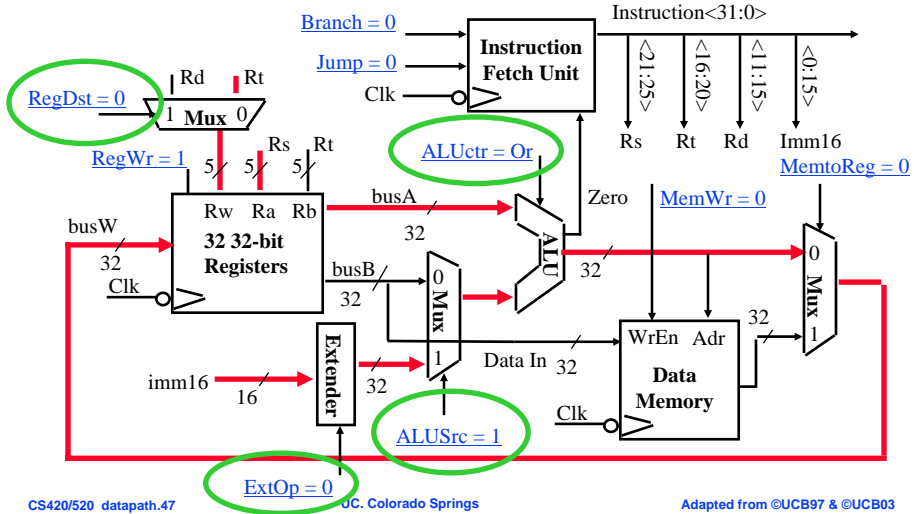◦  $R[rt] \leftarrow R[rs] \text{ or } \text{ZeroExt}[\text{Imm16}]$




CS420/520 datapath.47


UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

## The Single Cycle Datapath during Load

 

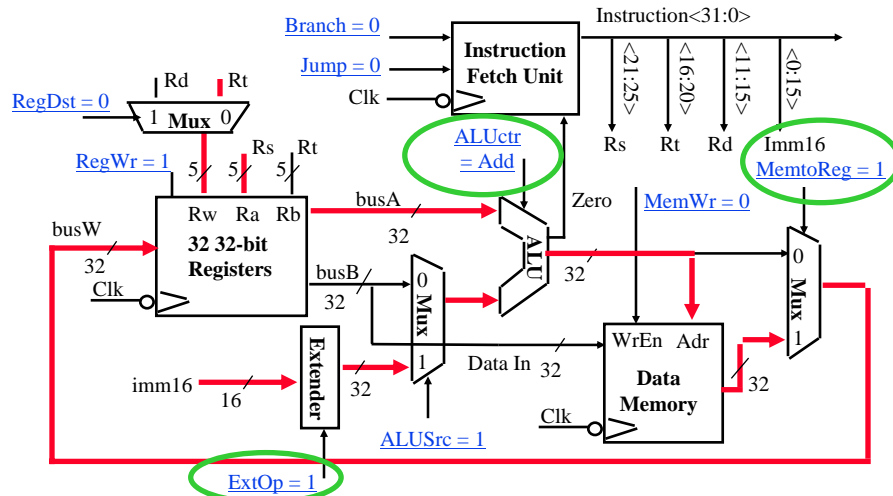◦  $R[rt] \leftarrow \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




CS420/520 datapath.48

UC, Colorado Springs


Adapted from ©UCB97 & ©UCB03


 
## The Single Cycle Datapath during Store



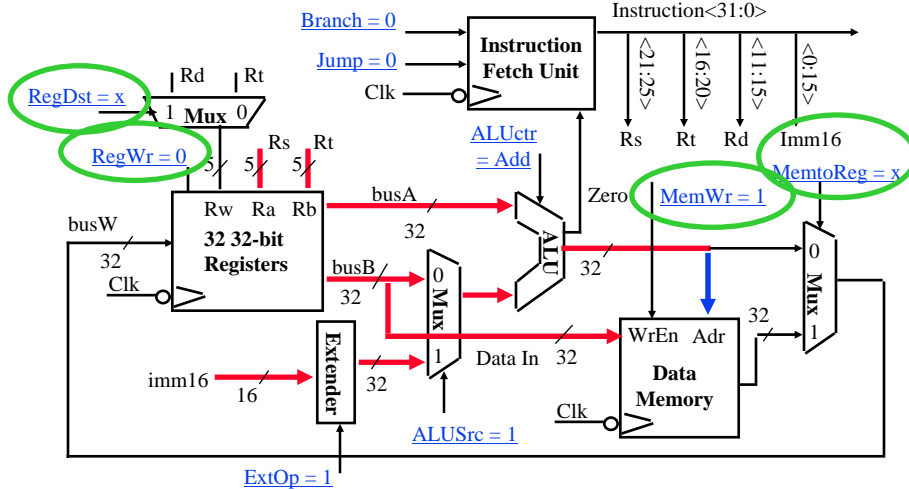◦ Data Memory  $\{R[rs] + \text{SignExt}[imm16]\} \leftarrow R[rt]$




CS420/520 datapath.49


UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03
 
## The Single Cycle Datapath during Branch



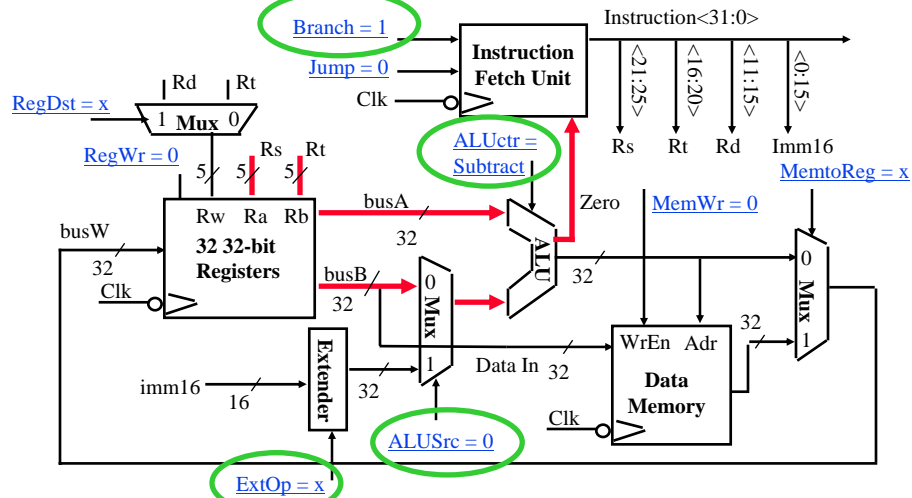◦ if  $(R[rs] - R[rt] == 0)$  then Zero  $\leftarrow 1$ ; else Zero  $\leftarrow 0$




CS420/520 datapath.50


UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03
 
## Instruction Fetch Unit at the End of Branch



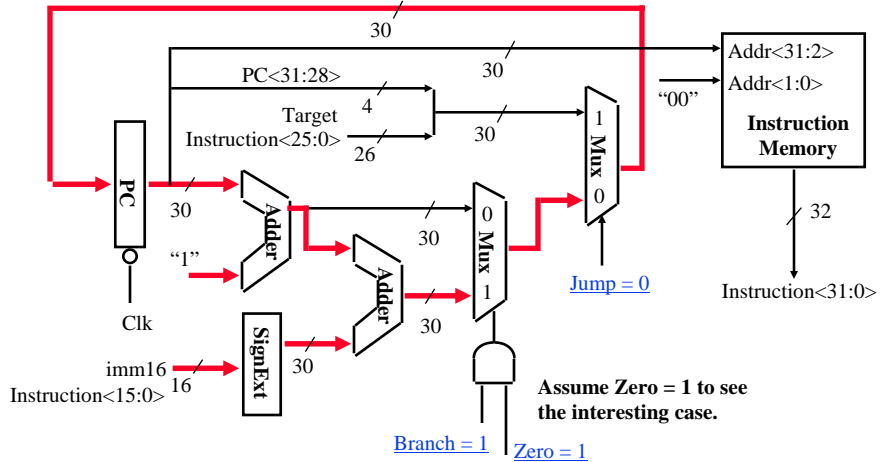◦ if (Zero == 1) then PC = PC + 4 + SignExt[imm16]\*4 ; else PC = PC + 4



CS420/520 datapath.51


UC. Colorado Springs

Adapted from ©UCB97 & ©UCB03
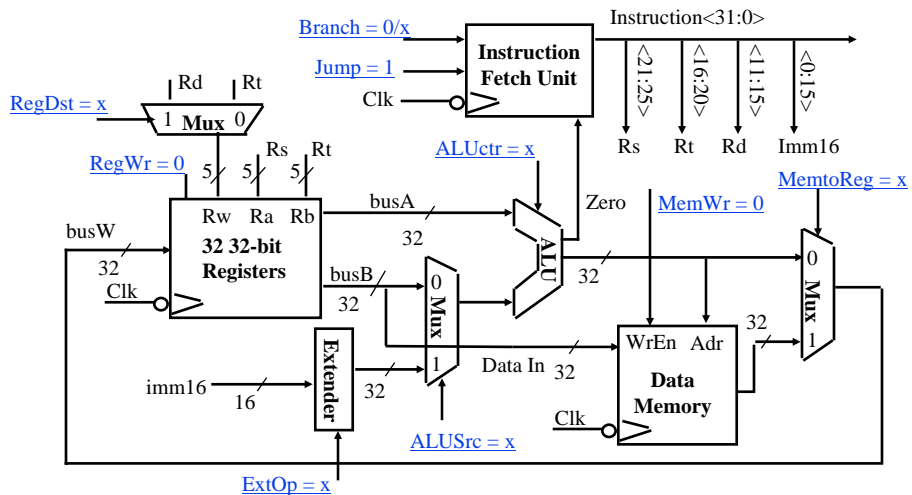
## The Single Cycle Datapath during Jump



◦ Nothing to do! Make sure control signals are set correctly!




CS420/520 datapath.52


UC. Colorado Springs

Adapted from ©UCB97 & ©UCB03

 
## Instruction Fetch Unit at the End of Jump



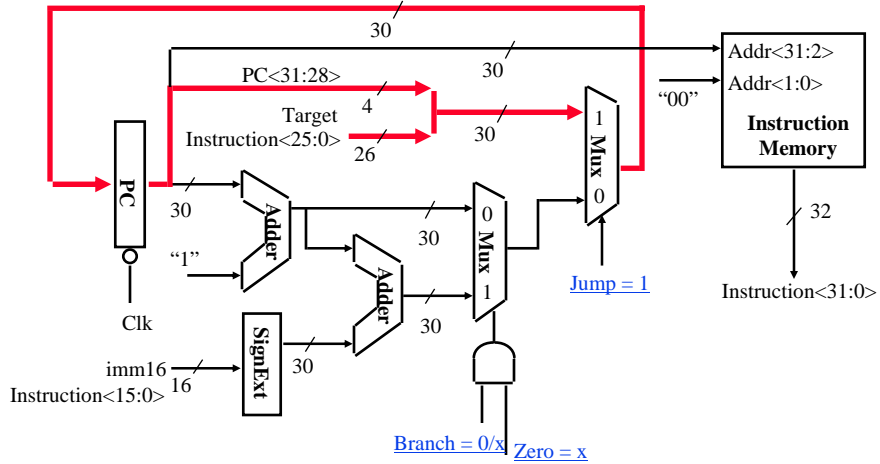
° PC ← PC<31:28> concat target<25:0> concat “00”



## Step 4: Given Datapath: ---> Control

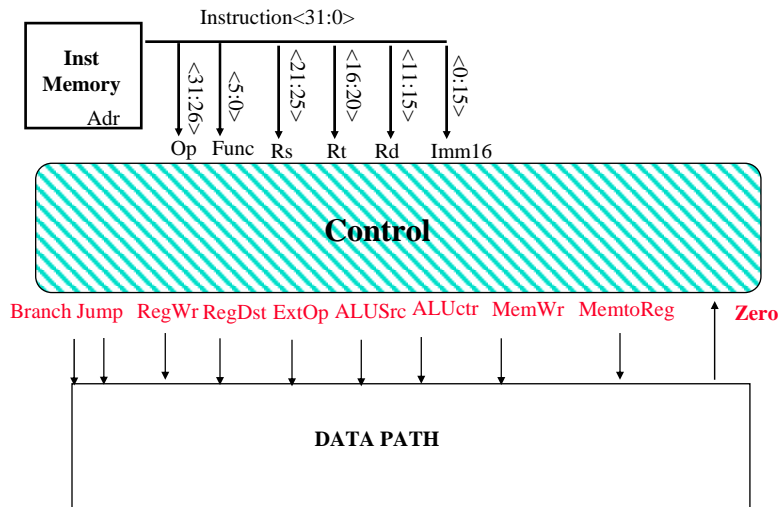
 
## The "Truth Table" for the Main Control



op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUOp (Symbolic)	"R-type"	Or	Add	Add	Subtract	xxx
ALUOp <2>	1	0	0	0	0	x
ALUOp <1>	0	1	0	0	0	x
ALUOp <0>	0	0	0	0	1	x

CS420/520 datapath.55

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

## The "Truth Table" for RegWrite


op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegWrite	1	1	1	0	0	0

° RegWrite = R-type + ori + lw

= !op<5> & !op<4> & !op<3> & !op<2> & !op<1> & !op<0> (R-type)

+ !op<5> & !op<4> & op<3> & op<2> & !op<1> & op<0> (ori)

 + op<5> & !op<4> & !op<3> & !op<2> & op<1> & op<0> (lw)




CS420/520 datapath.56


UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

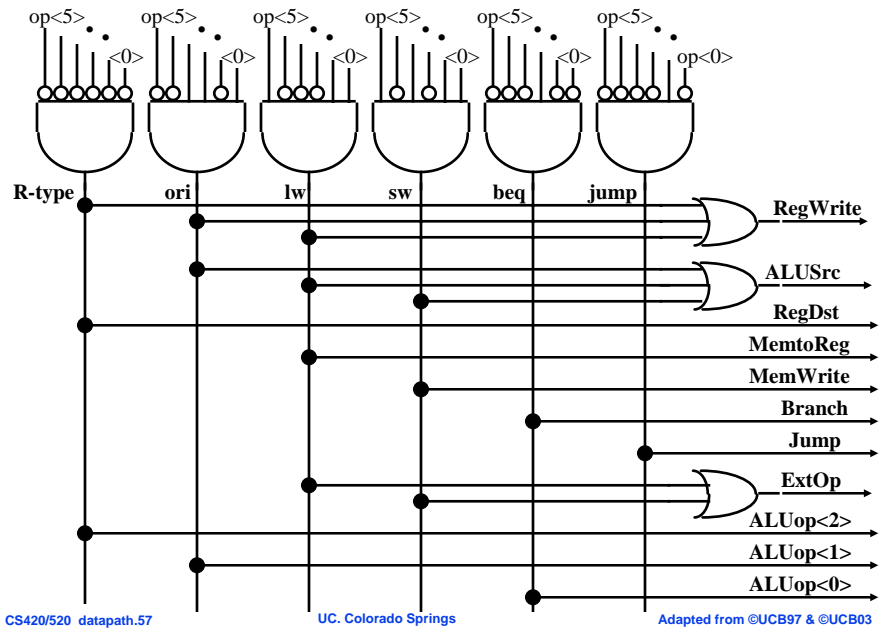
## PLA Implementation of the Main Control



 
## PLA Implementation of the Main Control: Drawing II


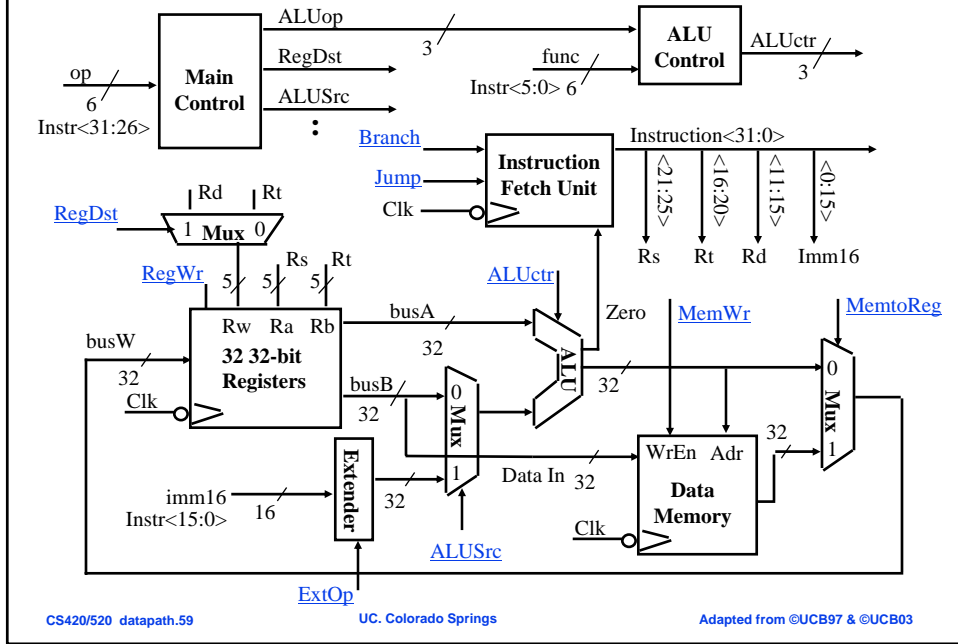
## Putting it All Together: A Single Cycle Processor


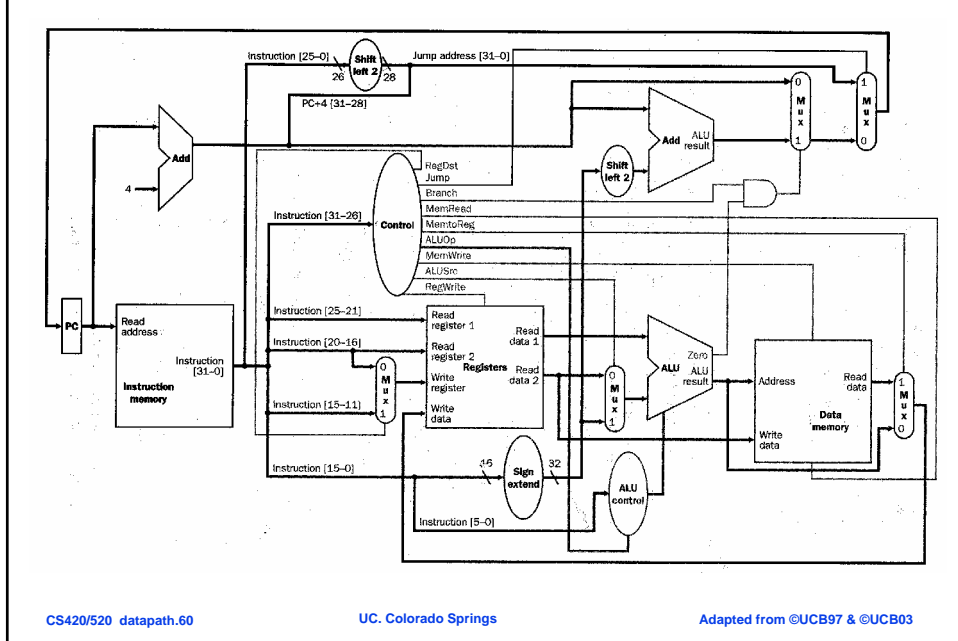
## Putting it All Together: An Extended View



## Where to get more information?

- CO2: Chapter 4.1 to 4.5 (pp.210 – 236); Chapter 5.1 to 5.3
- CO3: Chapter 3.1 – 3.3 (pp. 160 – 176); Chapter 5.1 to 5.4
  - David Patterson and John Hennessy, “Computer Organization & Design: The Hardware / Software Interface,” Morgan Kaufman Publishers; CO2 (2nd edition) and CO3 (3rd edition)
- One of the best PhD thesis on processor design:
  - Manolis Katevenis, “Reduced Instruction Set Computer Architecture for VLSI,” PhD Dissertation, EECS, U.C. Berkeley, 1982.
- For a reference on the MIPS architecture:
  - Gerry Kane, “MIPS RISC Architecture,” Prentice Hall.

## CO review: Two’s Complement Representation


- 2’s complement representation of negative numbers (**signed**)
  - Bitwise inverse and add 1
  - The MSB is always “1” for negative number => sign bit
- Biggest 4-bit Binary Number: 7      Smallest 4-bit Binary Number: -8

Decimal	Binary	Decimal	Bitwise Inverse (1’s Com.)	2’s Complement
0	0000	0	1111	0000
1	0001	-1	1110	1111
2	0010	-2	1101	1110
3	0011	-3	1100	1101
4	0100	-4	1011	1100
5	0101	-5	1010	1011
6	0110	-6	1001	1010
7	0111	-7	1000	1001
8	1000	-8	0111	1000

“Illegal” Positive Number!
 
## CO review: A One-bit Full Adder

- This is also called a (3, 2) adder
- Half Adder: No CarryIn nor CarryOut
- Truth Table:



Inputs			Outputs		Comments
A	B	CarryIn	CarryOut	Sum	
0	0	0	0	0	0 + 0 + 0 = 00
0	0	1	0	1	0 + 0 + 1 = 01
0	1	0	0	1	0 + 1 + 0 = 01
0	1	1	1	0	0 + 1 + 1 = 10
1	0	0	0	1	1 + 0 + 0 = 01
1	0	1	1	0	1 + 0 + 1 = 10
1	1	0	1	0	1 + 1 + 0 = 10
1	1	1	1	1	1 + 1 + 1 = 11


CS420/520 datapath.63

UC, Colorado Springs


Adapted from ©UCB97 & ©UCB03

## CO review: Logic Diagrams for CarryOut

- $\text{CarryOut} = (B \ \& \ \text{CarryIn}) \ | \ (A \ \& \ \text{CarryIn}) \ | \ (A \ \& \ B)$

 

 - $\text{Sum} = A \ \text{XOR} \ B \ \text{XOR} \ \text{CarryIn}$



CS420/520 datapath.64



UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03


  
## CO review: Overflow Detection

- **Overflow: the result is too large (or too small) to represent properly**
  - Example:  $-8 < \leq$  4-bit binary number  $\leq 7$
- **When adding operands with different signs, overflow cannot occur!**
- **Overflow occurs when adding:**
  - 2 positive numbers and the sum is negative
  - 2 negative numbers and the sum is positive
- **Optional homework exercise: Prove you can detect overflow by:**
  - Carry into MSB  $\neq$  Carry out of MSB




CS420/520 datapath.65

UC. Colorado Springs

Adapted from ©UCB97 & ©UCB03
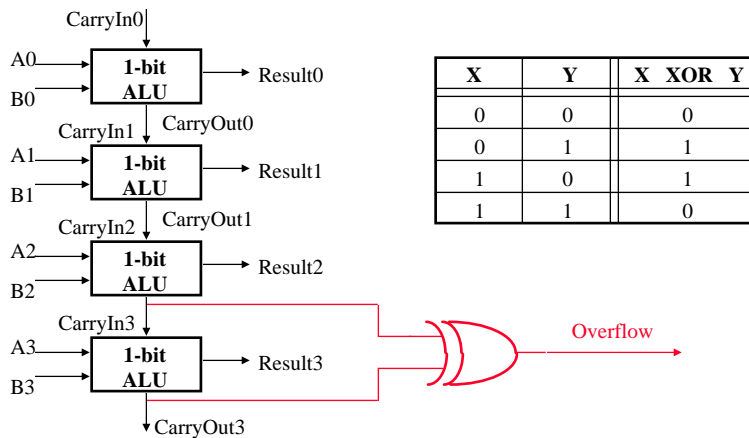
## CO review: Overflow Detection Logic

- **Carry into MSB  $\neq$  Carry out of MSB**
  - For a N-bit ALU:  $\text{Overflow} = \text{CarryIn}[N - 1] \text{ XOR } \text{CarryOut}[N - 1]$



CS420/520 datapath.66

UC. Colorado Springs

Adapted from ©UCB97 & ©UCB03