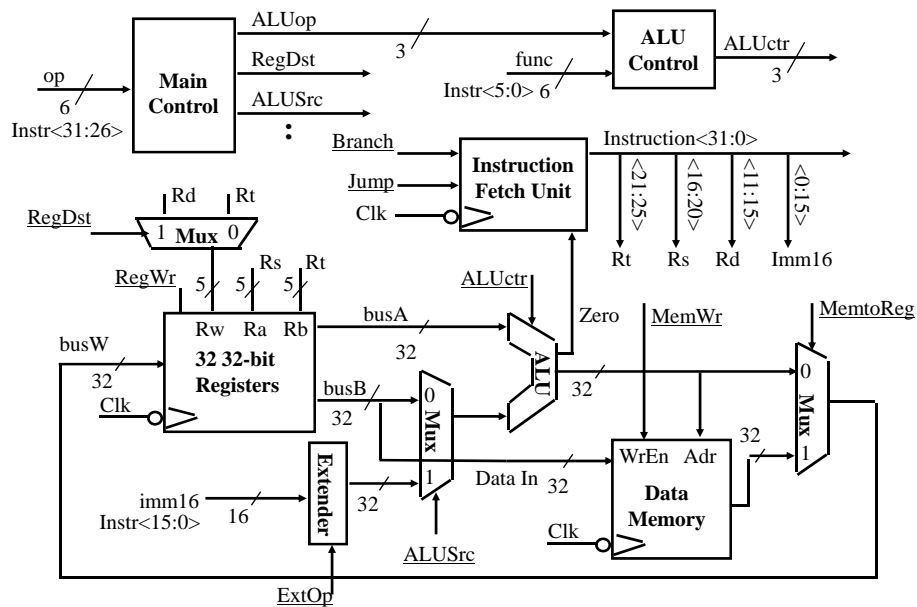


CS420/520 Computer Architecture I


Designing a Multiple Cycle Processor

Dr. Xiaobo Zhou
Department of Computer Science

Review: A Single Cycle Processor



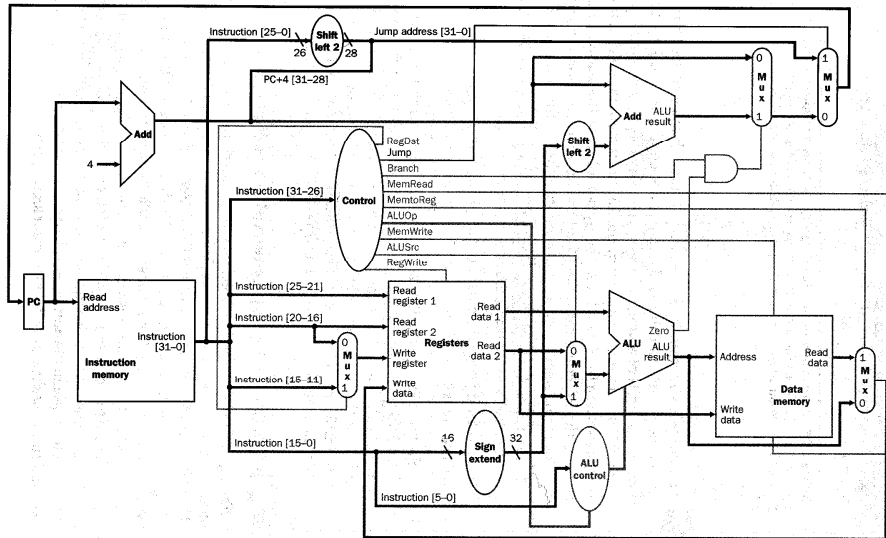Review: Putting it All Together: An Extended View



CS420/520 multipath...3

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

Drawbacks of this Single Cycle Processor

- Long cycle time:
 - Cycle time must be long enough for the load instruction:
 - Instruction Memory Access Time +
 - Register File Access (Reading) Time +
 - ALU Delay (address calculation) +
 - Data Memory Access Time +
 - Register File Setup & Writing Time
- Cycle time is much longer than needed for all other instructions.

Examples:

 - R-type instructions do not require data memory access
 - Jump does not require ALU operation nor data memory access

CS420/520 multipath...4

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03


Performance Comparisons

- Assume that the operation times for the major functional units in a single cycle implementation are the following
 - Memory units: 2 ns
 - ALU and Adders: 2ns
 - Register file (read or write): 1 ns
 - The multiplexors, control unit, PC accesses, sign extension unit, and wires have no delay.
- Questions: which of the following implementations would be faster, and by how much?
 - A fixed-single-cycle implementation
 - A *flexible*-single-cycle implementation: using a variable-length clock, which for each instruction is only as long as it needs to be
- To compare, assume the following instruction mix:
 - 24% loads, 12% stores, 44% ALUs, 20% branches

Overview of a Multiple Cycle Implementation

- The root of the single cycle processor's problems:
 - The cycle time has to be long enough for the slowest instruction
- Solution:
 - Break the instruction into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
 - Cycle time: time it takes to execute the longest step
 - Keep all the steps to have similar length
 - This is the essence of the multiple cycle processor
- The advantages of the multiple cycle processor:
 - Cycle time is much shorter
 - Different instructions take different number of cycles to complete
 - Load takes five cycles
 - Reg-type only takes four cycles; Jump 3; Branch 3 or 4
 - **Allows a functional unit to be used more than once per instruction**
 - Adder + ALU
 - Instruction mem + Data mem

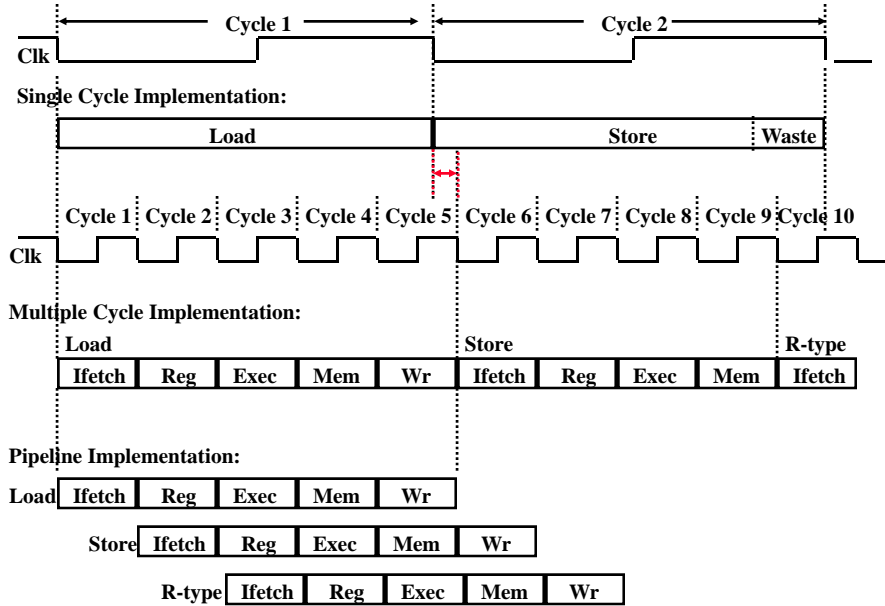Single Cycle, Multiple Cycle, vs. Pipeline



CS420/520 multipath..7

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

Performance Comparisons (Cont.)

- Assume that the operation times for the major functional units in a single cycle implementation are the following
 - Memory units: 2 ns
 - ALU and Adders: 2ns
 - Register file (read or write): 1 ns
 - The multiplexors, control unit, PC accesses, sign extension unit, and wires have no delay.
- Questions: which of the following implementations would be faster, and by how much?
 - A fixed-single-cycle implementation
 - A *flexible*-single-cycle implementation: using a variable-length clock, which for each instruction is only as long as it needs to be
 - **A multiple-cycle implementation**
- To compare, assume the following instruction mix:
 - 24% loads, 12% stores, 44% ALUs, 20% branches

CS420/520 multipath..8

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

Instruction Executions on a Multi-Cycle Datapath (BEQZ)


- In theory, you need a register to hold a signal value if:
 - (1) The signal is computed in one clock cycle and used in another.
- Instruction Fetch Cycle (IF)
 - $IR \leftarrow Mem[PC]$; $NPC \leftarrow PC + 4$
- Instruction Decode / Register Fetch (ID/RF)
 - $A \leftarrow Reg[rs]$; $B \leftarrow Reg[rt]$; $Imm \leftarrow Sign-Ext(Imm\ 16)$
- Execution (EXEC)
 - Mem reference (Load/Store): $ALUOutput \leftarrow A + Imm$
 - Reg-Reg ALU: $ALUOutput \leftarrow A\ op\ B$; or Reg-Imm ALU: $A\ op\ Imm$
 - **BEQZ**: $ALUOutput \leftarrow NPC + (Imm \ll 2)$; $Cond \leftarrow (A == 0)$
- Memory access / BEQZ completion (MEM)
 - Memory reference (Load): $LMD \leftarrow Mem[ALUoutput]$
 - Memory reference (Store): $Mem[ALUoutput] \leftarrow B$
 - BEQZ: if (Cond) $PC \leftarrow ALUOutput$
- Write-back cycle(WB)
 - Reg-Reg ALU: $Reg[rd] \leftarrow ALUOutput$; or Reg-Imm ALU: $Reg[rt] \leftarrow ALUOutput$
 - Load: $Reg[rt] \leftarrow LMD$

CS420/520 multipath..9

UC. Colorado Springs

Adapted from ©UCB97 & ©UCB03

An Idealized Multiple Cycle Datapath

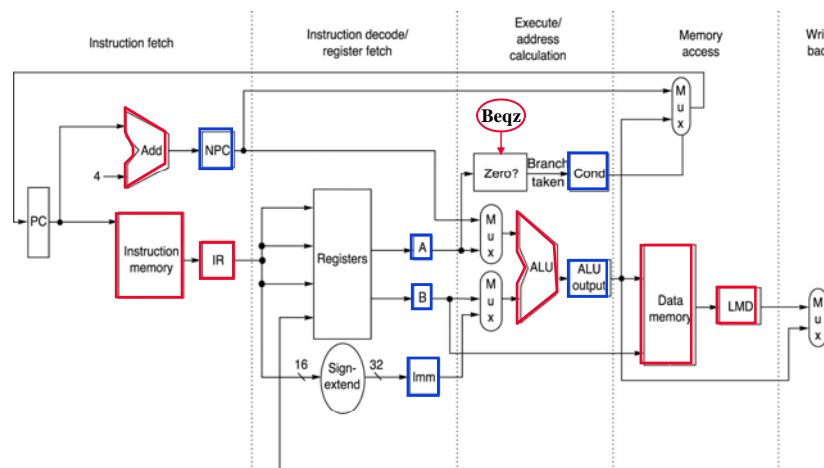

- **Allows a functional unit to be used more than once per instruction**
 - Adder + ALU
 - Instruction mem + Data mem

CS420/520 multipath..10

© 2003 Elsevier Science (USA). All rights reserved.
UC. Colorado Springs

Adapted from ©UCB97 & ©UCB03



Revisit Instruction Executions (in case of BEQ)

Step Name	Action for R-type instructions	Action for memory-reference instructions	Action for Branches	Action for Reg-Imme
Instruction Fetch	IR = Mem[PC], PC = PC + 4			
Instruction decode/ Register fetch	A = Reg [IR[25:21]] B = Reg [IR[20:16]] Target \leftarrow ALUout = PC + (sign-extend (IR[15:0]) << 2)			
Execution, address computation, branch /jump completion	ALUout = A op B	ALUout = A + sign-extend (IR[15:0])	If (A == B) then PC = Target	ALUout = A op Imme
Memory access		Load : Data-out = Mem[ALUout] or Store : Mem[ALUout] = B		
Write-back	Reg [IR[15:11]] = ALUout	Load : Reg [IR[20:16]] = Data-out		Reg [IR[20:16]] = ALUout

Control signals have to be set *per-Step*, instead of per instruction in single cycle datapath!

Instruction Fetch Cycle: In the Beginning

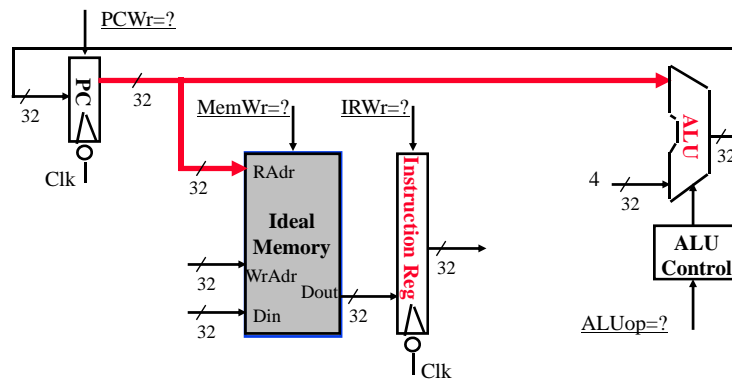 
- Every cycle begins right AFTER the clock tick:
 - mem[PC] PC<31:0> + 4



Instruction Fetch Cycle: The End

Every cycle ends AT the next clock tick (storage element updates):

- IR ← mem[PC] PC<31:0> ← PC<31:0> + 4

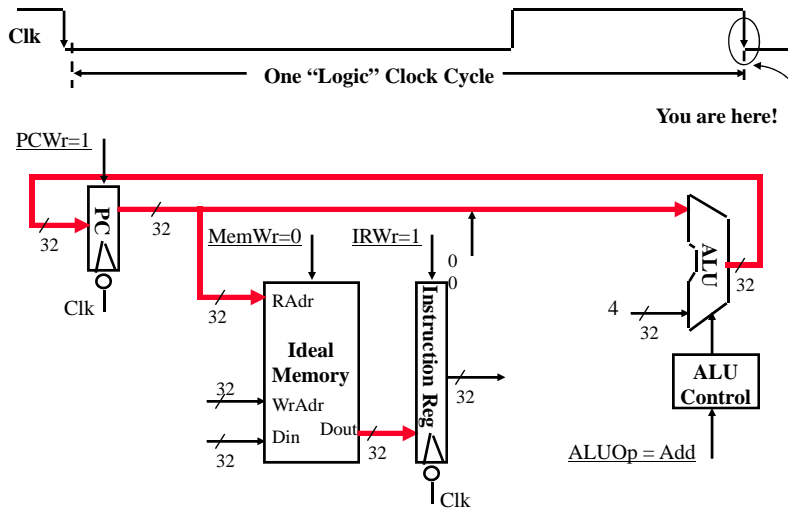

CS420/520 multipath..13


UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

Instruction Fetch Cycle: Overall Picture

Ifetch

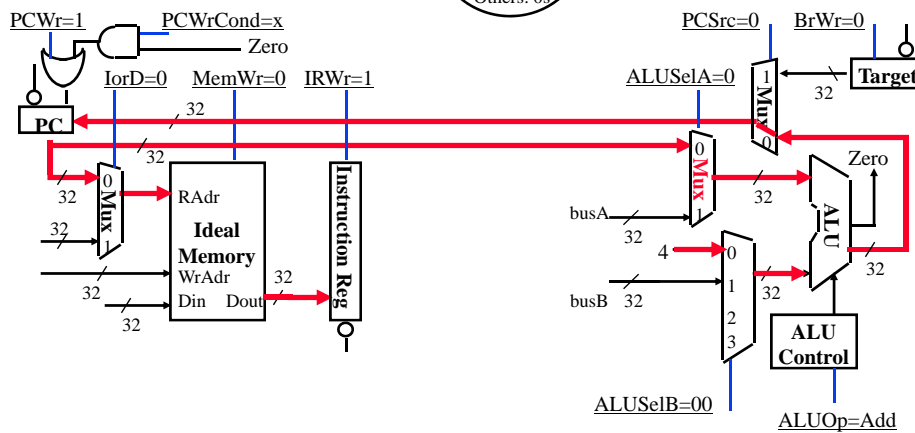ALUOp=Add
1: PCWr, IRWr
x: PCWrCond
RegDst, Mem2R
Others: 0s




CS420/520 multipath..14

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

Putting it all together: Multiple Cycle Datapath

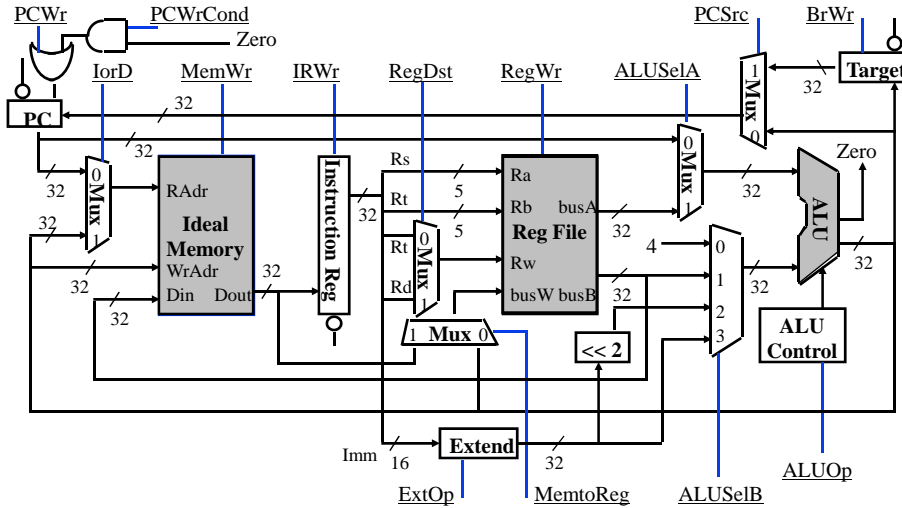- MCP: A functional unit to be used more than once per instruction
 - Not good for pipelining




CS420/520 multipath..15

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

A Multiple Cycle Delay Path

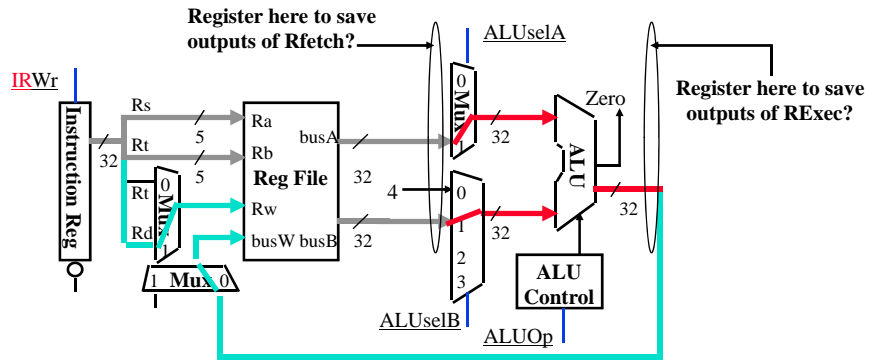- There is no register to save the results between:
 - Register Fetch: busA \leftarrow Reg[rs] ; busB \leftarrow Reg[rt] ———
 - R-type Execution: ALU output \leftarrow busA op busB ———
 - R-type Completion: Reg[rd] \leftarrow ALU output ———



CS420/520 multipath..16

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

A Multiple Cycle Delay Path (Continue)

- Register is NOT needed to save the outputs of Register Fetch:
 - IRWr = 0: busA and busB will not change after Register Fetch
- Register is NOT needed to save the outputs of R-type Execution:
 - busA and busB will not change after Register Fetch
 - Control signals ALUSelA, ALUSelB, and ALUOp will not change after R-type Execution
 - Consequently ALU output will not change after R-type Execution
- In theory, you need a register to hold a signal value if:
 - (1) The signal is computed in one clock cycle and used in another.
 - (2) AND the inputs to the functional block that computes this signal can change before the signal is written into a state element.
- You can save a register if Cond 1 is true BUT Cond 2 is false:
 - But in practice, this will introduce a multiple cycle delay path:
 - A logic delay path that takes multiple cycles to propagate from one storage element to the next storage element


CS420/520 multipath..17

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

Instruction Fetch Cycle

◦ $IR \leftarrow mem[PC]; PC = PC + 4$

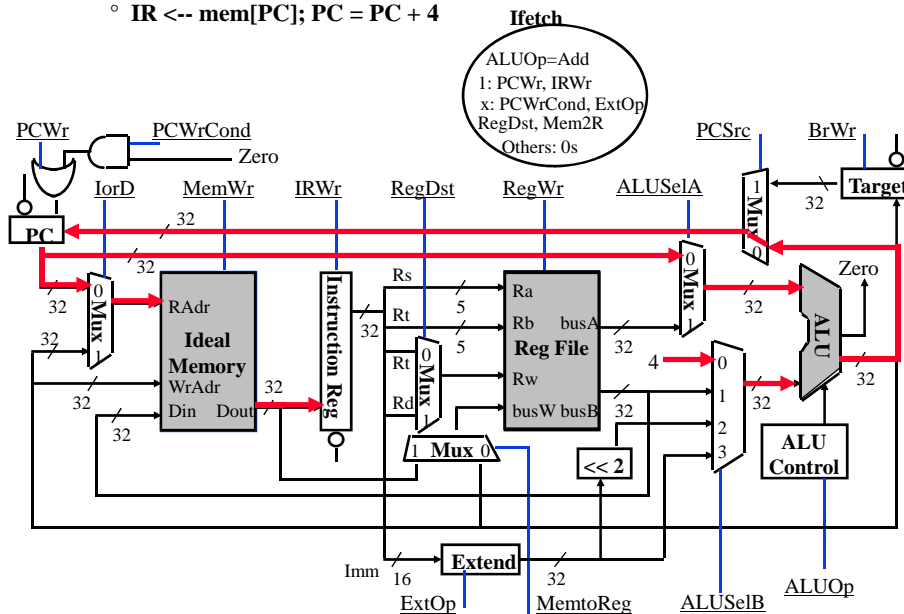

CS420/520 multipath..18

UC, Colorado Springs


Adapted from ©UCB97 & ©UCB03

Register Fetch / Instruction Decode (Continue)

- busA <- Reg[rs] ; busB <- Reg[rt] ;
- Target <- PC + SignExt(Imm16)*4
(speculative calculation)

Rfetch/Decode

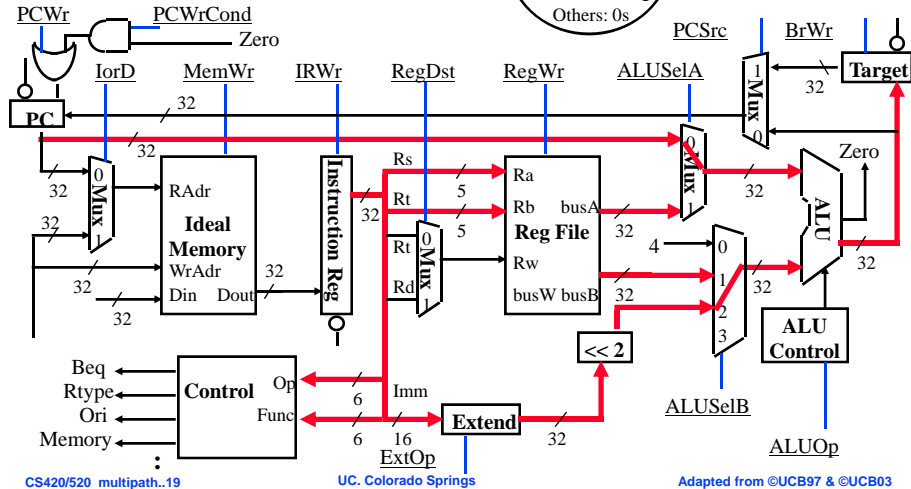ALUOp=Add
 1: BrWr, ExtOp
 ALUSelB=10
 x: RegDst, PCSrc
 IorD, MemtoReg
 Others: 0s




Instruction Decode: We have a Branch!

- if (busA == busB)
 - PC <- Target
 - **But could be a long cycle time**

BrComplete

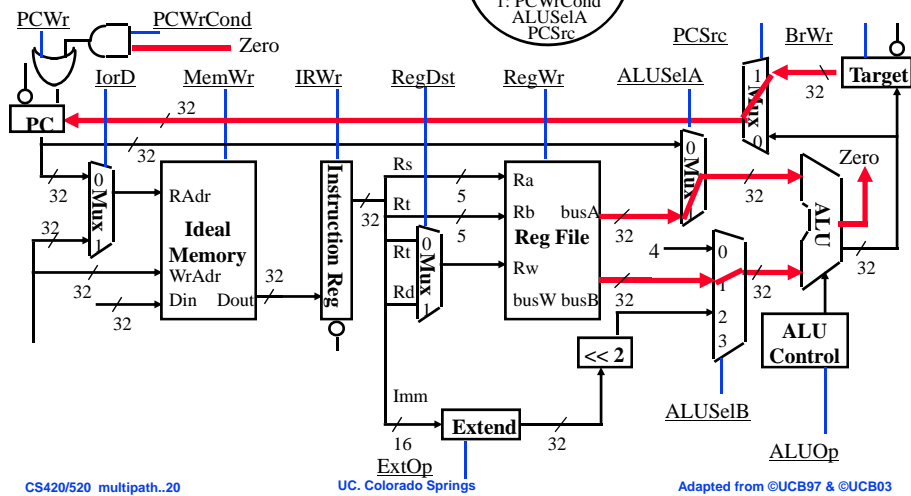ALUOp=Sub
 ALUSelB=01
 x: IorD, Mem2Reg
 RegDst, ExtOp
 1: PCWrCond
 ALUSelA
 PCSrc




Instruction Decode: We have a R-type!

ALU Output \leftarrow busA op busB

RExec

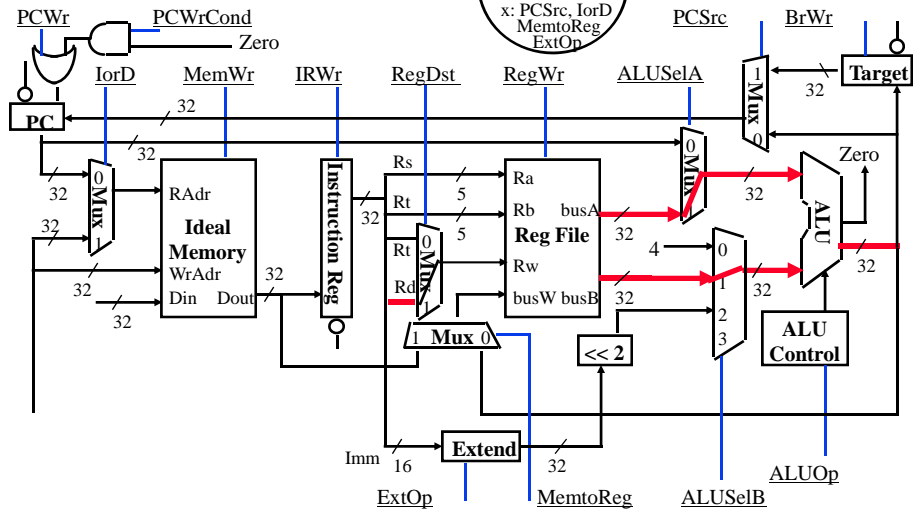1: RegDst
ALUSelA
ALUSelB=01
ALUOp=Rtype
x: PCSrc, IorD
MemtoReg
ExtOp



CS420/520 multipath..21

UC, Colorado Springs


Adapted from ©UCB97 & ©UCB03

R-type Completion

R[rd] \leftarrow ALU Output

Rfinish

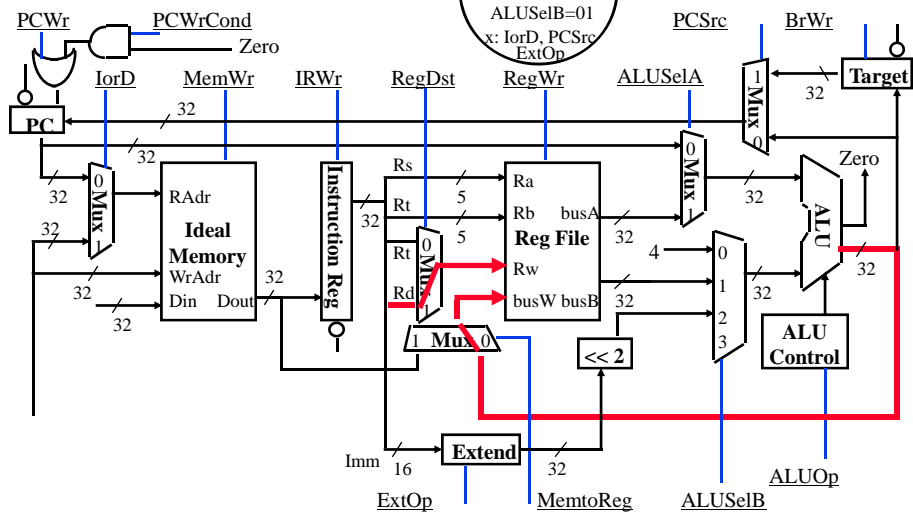ALUOp=Rtype
1: RegDst, RegWr
ALUSelA
ALUSelB=01
x: IorD, PCSrc
ExtOp



CS420/520 multipath..22


UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

Instruction Decode: We have an Ori!

- ALU output \leftarrow busA or ZeroExt[Imm16]

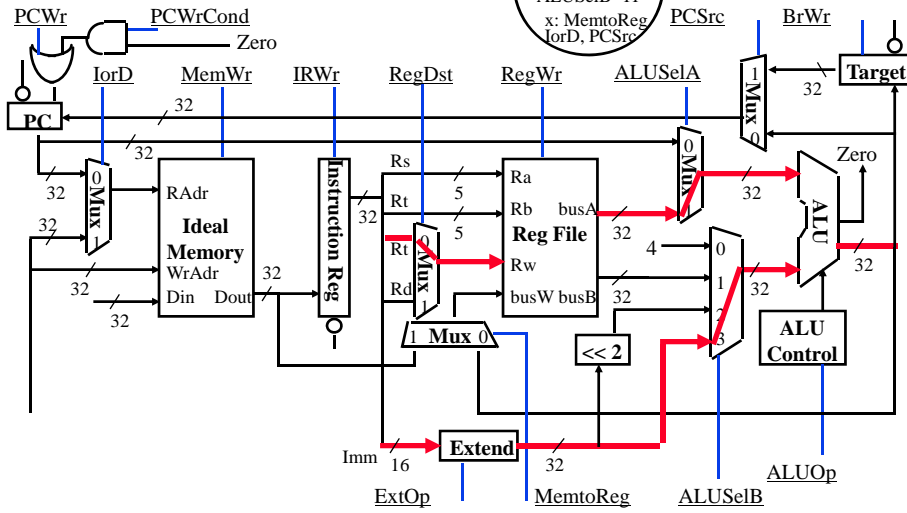
OriExec
 ALUOp=Or
 1: ALUSelA
 ALUSelB=11
 x: MemtoReg
 IorD, PCSrc



Ori Completion


- Reg[rt] \leftarrow ALU output

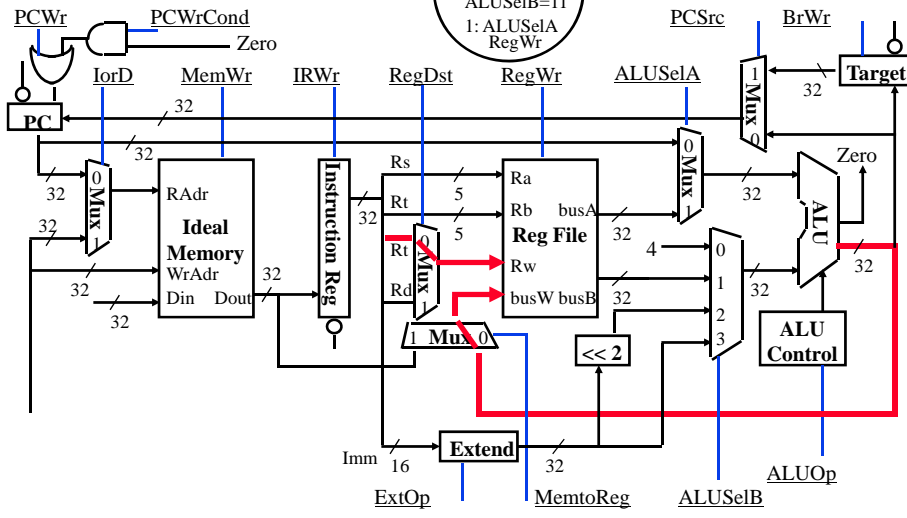OriFinish
 ALUOp=Or
 x: IorD, PCSrc
 ALUSelB=11
 1: ALUSelA
 RegWr




Instruction Decode: We have a Memory Access!

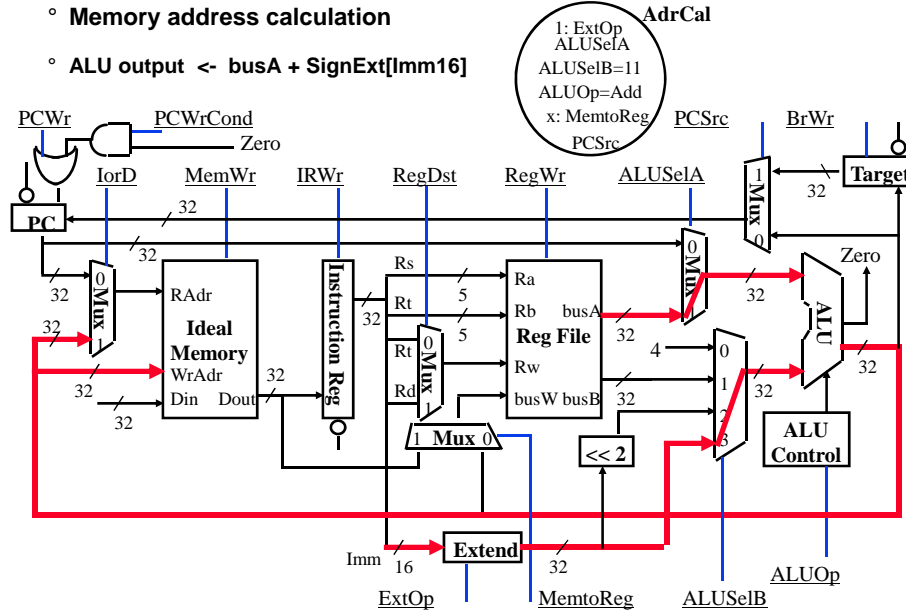- Memory address calculation
- ALU output \leftarrow busA + SignExt[Imm16]




Memory Access for Store

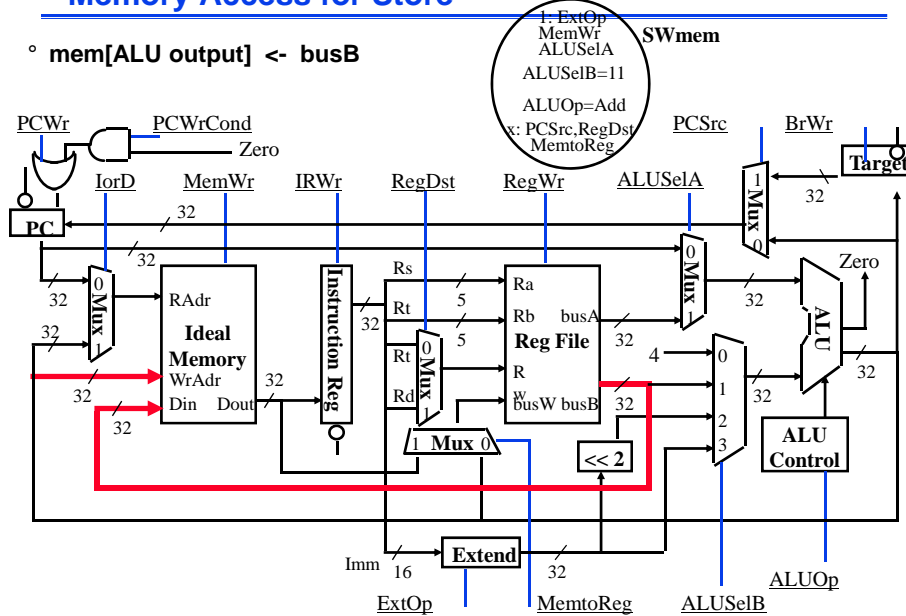- $\text{mem}[\text{ALU output}] \leftarrow \text{busB}$




Memory Access for Load

◦ Mem Dout ← mem[ALU output]

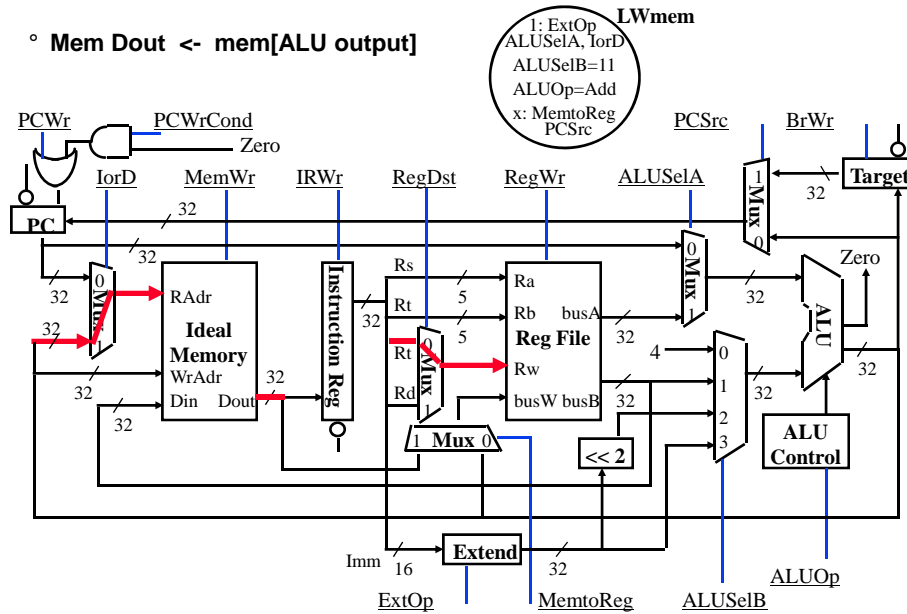


Write Back for Load

◦ Reg[rt] ← Mem Dout

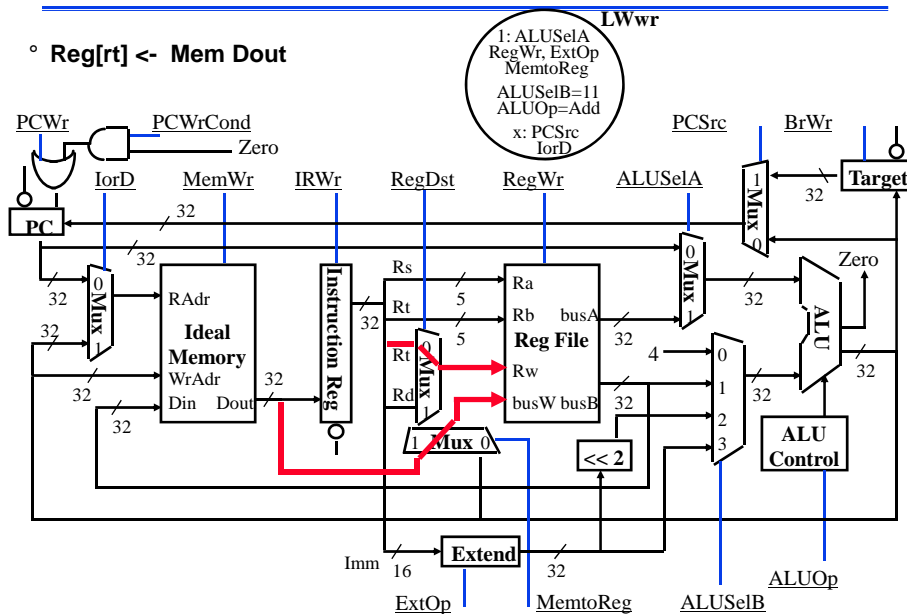

Putting it all together: Multiple Cycle Datapath

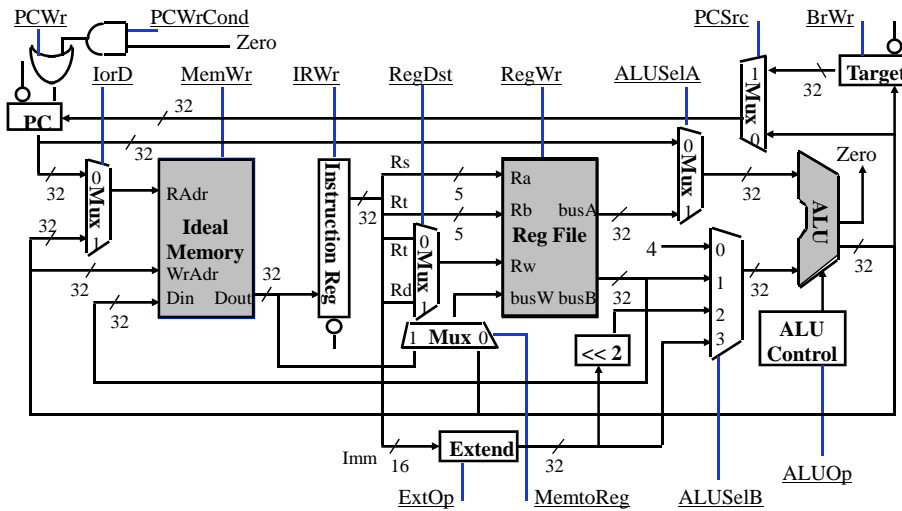- MCP: A functional unit to be used more than once per instruction
- Not good for pipelining




CS420/520 multipath..29

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

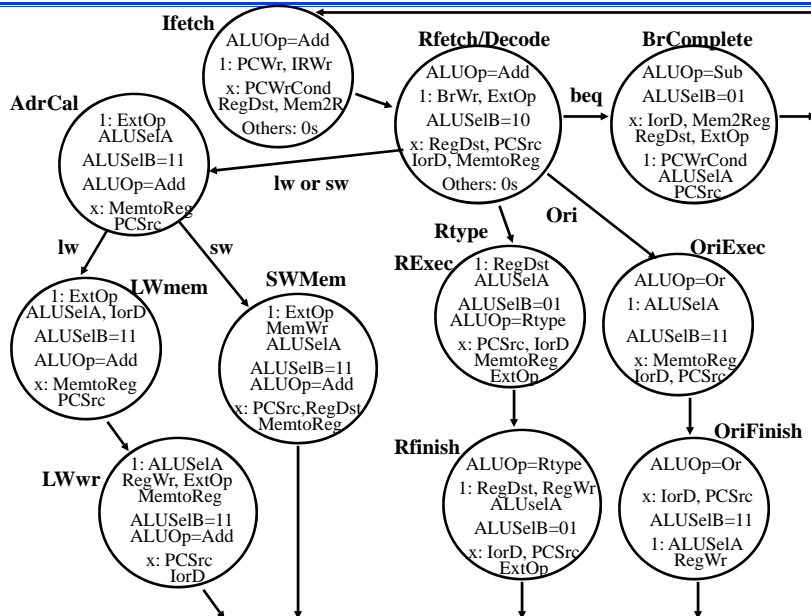Putting it all together: Control State Diagram



CS420/520 multipath..30

UC, Colorado Springs

Adapted from ©UCB97 & ©UCB03

Summary

- **Disadvantages of the Single Cycle Processor**
 - Long cycle time
 - Cycle time is too long for all instructions except the Load
- **Multiple Cycle Processor:**
 - Divide the instructions into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
- **Do NOT confuse Multiple Cycle Processor w/ Multiple Cycle Delay Path**
 - Multiple Cycle Processor executes each instruction in multiple clock cycles
 - Multiple Cycle Delay Path: a combinational logic path between two storage elements that takes more than one clock cycle to complete
- **It is possible (desirable) to build a MC Processor without MCDP:**
 - Use a register to save a signal's value whenever a signal is generated in one clock cycle and used in another cycle later
- **More reading:** CA3/4: A26-A30, CO2 (Ch 5.4); CO3 (Ch 5.5)